

Combinational Circuit Design using VHDL and FPGAs

Project 3

Design and In-Circuit Verification of a 16-bit ALU

ALU Design Specifications

An Arithmetic Logic Unit (ALU) is a combinational circuit that performs arithmetic and logical operations. **Figure 1** shows the specifications of the 16-bit ALU that will be implemented in this project.

Inputs :	A, B, S_OP		
Outputs :	RES, COUT, VOUT		
Behavior-Functionality			
S_OP (4 bits)	RES (16 bits)	COUT (1 bit)	VOUT (1 bit)
0000	A+B	Carry from the msb of the result	Two's complement overflow
0001	A-B	Logic 1 only if B>A, else logic 0	Two's complement overflow
0010	A XOR B	Z	Z
0011	A AND B	Z	Z
0100	A OR B	Z	Z
0101	LSL (A)	Z	Z
0110	LSR (A)	Z	Z
0111	ROL (A)	Z	Z
1000	ROR (A)	Z	Z
1001	ASR (A)	Z	Z
1010	SWAP (A)	Z	Z
OTHERS	Z	Z	Z
Notes :			
LSL : 1-bit Logical Shift Left LSR : 1-bit Logical Shift Right ROL : 1-bit Rotate Left ROR : 1-bit Rotate Right ASR : 1-bit Arithmetic Shift Right SWAP : Swap half words			
Z represents high impedance			

Figure 1

Inputs A and B are the 16-bit operands. Input S_OP is the select operation signal. Output signals value depends on S_OP signal's value as shown in **Figure 1**. For example when S_OP signal's value is equal to 0000, RES signal's value is equal to A+B, COUT signal's value is equal to the carry from

the msb of the result and VOUT signal's value is equal to the two's complement overflow.

Design and In-Circuit Verification of a 16-bit ALU

The following pages will demonstrate how to implement and verify in-circuit a 16-bit ALU using Xilinx ISE 13.3, VHDL and CORE Generator system as design entry, Xilinx Evaluation boards and ChipScope Pro tool for in-circuit verification.

1. Open Xilinx ISE :

Double click the ISE desktop icon. Alternatively open a new terminal and give the command `“./bin/ise”` (without the quotes). For remote users, open a new terminal and give the following commands `“export DISPLAY=:1”` and `“./remote/ise”` (without the quotes).

2. Create a new Xilinx ISE Project :

In the ISE Project Navigator window, select `File->New Project...` In the New Project Wizard window, type `Project3src` in the **Name** field and `/home/fpga-user/Documents/Project3src` in the **Location** field and click **Next** (see **Figure 2**).

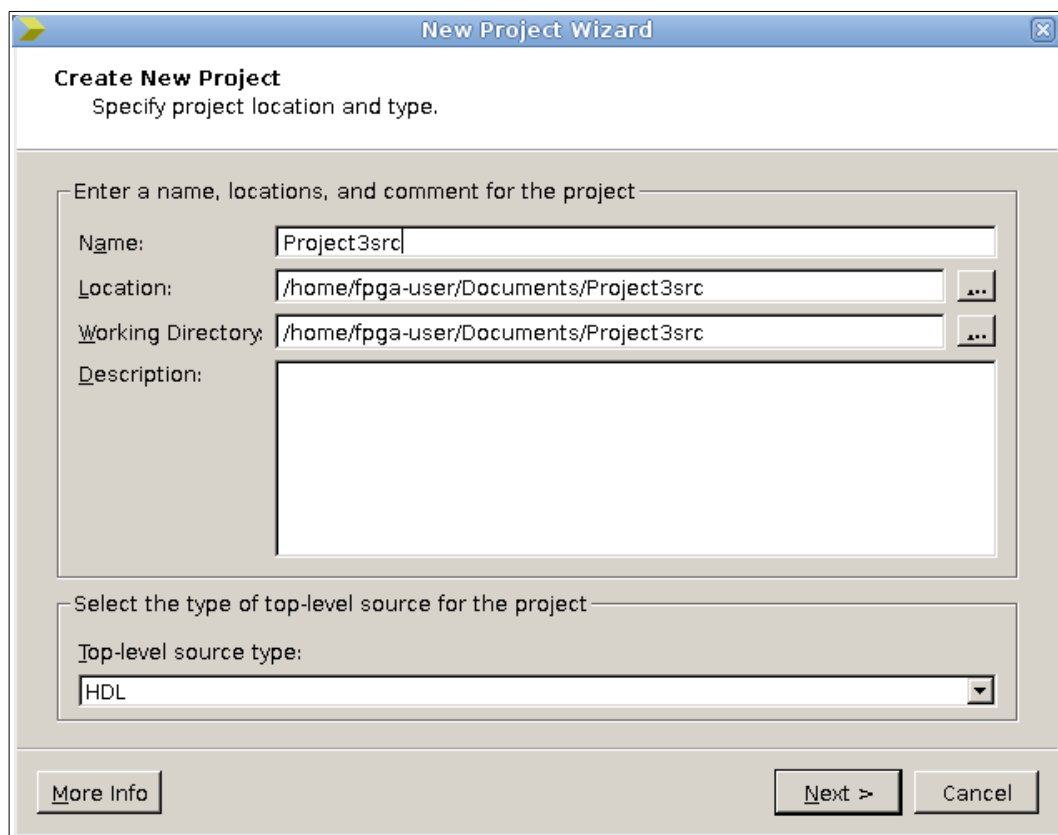


Figure 2

In the next New Project Wizard window, select the target Xilinx FPGA Evaluation board (e.g. the Spartan-6 SP605 Evaluation Platform) in the Evaluation Development Board field, select

VHDL in the Preferred Language field and click Next. The last New Project Wizard window must be similar to the one shown in **Figure 3**. Click Finish to create the project Project3src or navigate to the previous windows using Back to make corrections.

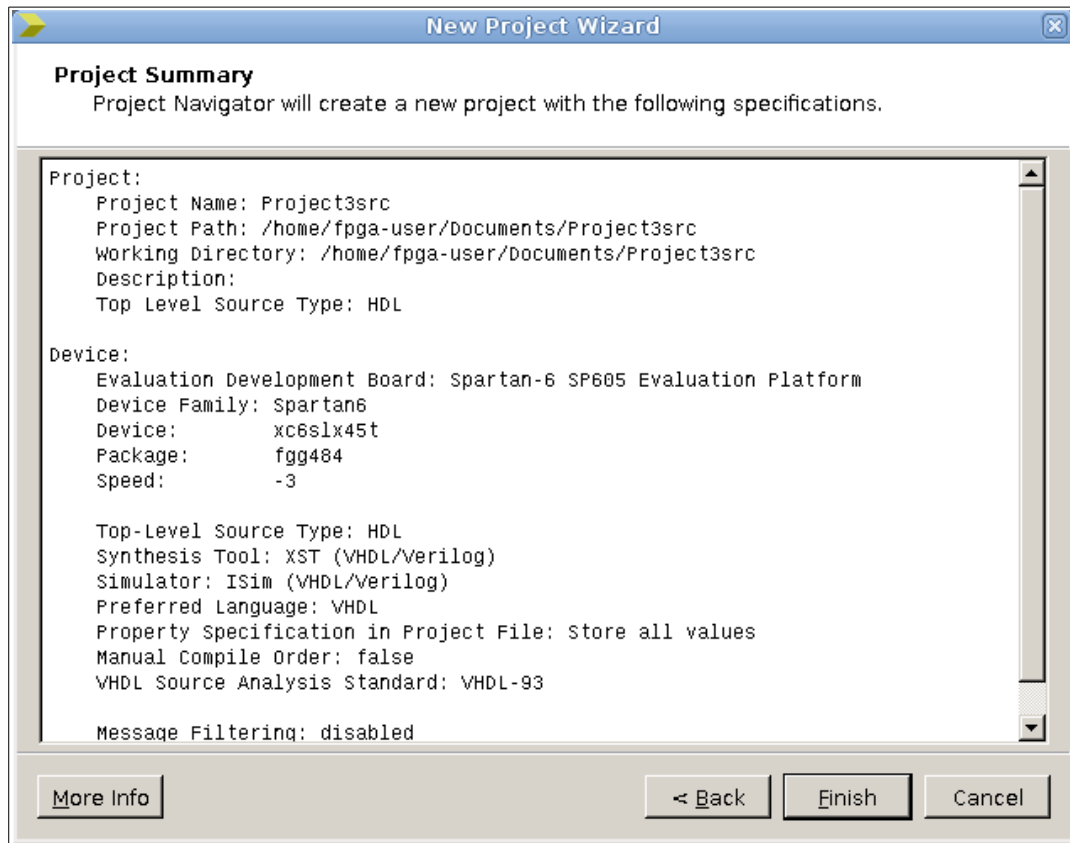


Figure 3

3. Add New Source in the Project3src project :

In the ISE Project Navigator window, select Project->New Source.... In the New Source Wizard window type alu_n in the File Name field, select VHDL Module and click Next (see **Figure 4**). The next New Source Wizard window must be completed as shown in **Figure 5**.

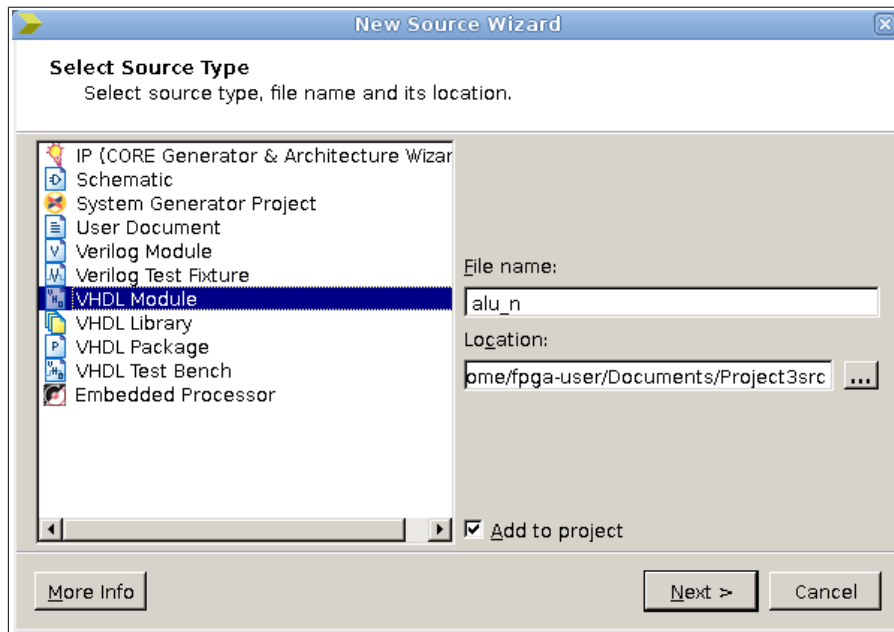


Figure 4

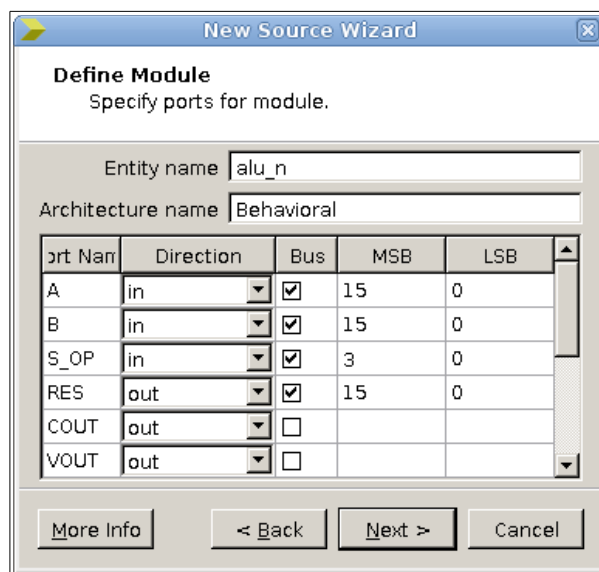


Figure 5

Clicking Next and Finish, the file `alu_n.vhd` is created.

4. Define the behavior of the `alu_n` VHDL module :

Remove the green highlighted lines (the comments) and edit the `alu_n.vhd` file to look like the one shown in Figure 6.

In Figure 6, line 5 states that the `NUMERIC_STD` package will be used. In this package the "+" operator is defined which is used to add signal values in the architecture body – to implement the $A+B$ and the $A-B$ operations.

In line 8 the `generic` statement is used to make the ALU description more general. The default value of the `N` parameter is 16, but this can easily change. The operators that are used to describe the parameterized length of a signal don't require any package statement (e.g. the “-” in the `(N-1 downto 0)` expression in line 9).

Lines 17-30 (architecture declarative region) define the signals used in the architecture body for internal circuit connections. The `cin` signal is of `integer` type. An `integer` signal represents a binary number. Using the `range` keyword the number of signal's bits can be declared (line 29). The `cin` signal's range is from 0 to 1. Integers in this range can be represented by one bit.

Lines 33-36 describe the $A+B$ and the $A-B$ operations. For example when `S_OP(0)='1'`, `tmp_b` signal's value is equal to `not B` and `cin` signal's value is equal to 1. In lines 35-36, after the required conversions, the values of signals `A`, `tmp_b` and `cin` are added. In this case $A+tmp_b+cin = A+(not\ B)+1 = A+(-B) = A-B$. When `S_OP(0)='0'`, `tmp_b` signal's value is equal to `B` and `cin` signal's value is equal to 0. In this case $A+tmp_b+cin = A+B+0 = A+B$.

```

1  -- PARAMETERIZED N-bit ALU.
2
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5  use IEEE.NUMERIC_STD.ALL;
6
7  entity alu_n is
8      generic(N : integer := 16);
9      Port(A,B : in  STD_LOGIC_VECTOR(N-1 DOWNT0 0);
10          S_OP : in  STD_LOGIC_VECTOR(3 DOWNT0 0);
11          RES : out STD_LOGIC_VECTOR(N-1 DOWNT0 0);
12          COUT : out STD_LOGIC;
13          VOUT : out STD_LOGIC);
14 end alu_n;
15
16 architecture Behavioral of alu_n is
17     signal add_op : STD_LOGIC_VECTOR(N DOWNT0 0);
18     signal xor_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
19     signal and_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
20     signal or_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
21     signal lsl_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
22     signal lsr_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
23     signal rol_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
24     signal ror_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
25     signal asr_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
26     signal swap_op : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
27
28     signal tmp_b : STD_LOGIC_VECTOR(N-1 DOWNT0 0);
29     signal cin : integer range 0 to 1;
30     signal bgta : STD_LOGIC;
31 begin
32     -- ADD,SUB OPERATIONS :
33     tmp_b <= (not B) when S_OP(0)='1' else B;
34     cin <= 1 when S_OP(0)='1' else 0;
35     add_op <= std_logic_vector(to_unsigned(to_integer(unsigned(A))
36         + to_integer(unsigned(tmp_b)) + cin,N+1));
37     -- REST OF THE OPERATIONS :
38     xor_op <= A xor B;
39     and_op <= A and B;
40     or_op <= A or B;
41     lsl_op <= A(N-2 downto 0) & '0';
42     lsr_op <= '0' & A(N-1 downto 1);
43     rol_op <= A(N-2 downto 0) & A(N-1);
44     ror_op <= A(0) & A(N-1 downto 1);
45     asr_op <= A(N-1) & A(N-1 downto 1);
46     swap_op <= A(N/2-1 downto 0) & A(N-1 downto N/2);
47     -- SELECT OPERATION MUX :
48     sel_op : process(S_OP,add_op(N-1 downto 0),xor_op,
49         and_op,or_op,lsl_op,lsr_op,rol_op,ror_op,asr_op,swap_op)
50     begin
51         case S_OP is
52             when "0000" => RES <= add_op(N-1 downto 0);
53             when "0001" => RES <= add_op(N-1 downto 0);
54             when "0010" => RES <= xor_op;
55             when "0011" => RES <= and_op;
56             when "0100" => RES <= or_op;
57             when "0101" => RES <= lsl_op;
58             when "0110" => RES <= lsr_op;
59             when "0111" => RES <= rol_op;
60             when "1000" => RES <= ror_op;
61             when "1001" => RES <= asr_op;
62             when "1010" => RES <= swap_op;
63             when OTHERS => RES <= (OTHERS => 'Z');
64         end case;
65     end process sel_op;
66     -- ONE'S AND TWO'S COMPLEMENT OVERFLOW :
67     bgta <= '1' when (unsigned(B) > unsigned(A)) else '0';
68     with S_OP select
69         COUT <= add_op(N) when "0000",
70             bgta when "0001",
71             'Z' when OTHERS;
72     VOUT <= ((A(N-1) and tmp_b(N-1) and (not add_op(N-1))) or
73         ((not A(N-1)) and (not tmp_b(N-1)) and add_op(N-1)))
74         when S_OP(3 downto 1)="000" else 'Z';
75 end Behavioral;

```

Figure 6

In lines 35-36 the “+” operator is used to add the values of A, tmp_b and cin signals. The A and tmp_b signal values are first converted to the unsigned type and then to the integer type. The type conversions are necessary because the “+” operator is not defined for signals of the STD_LOGIC_VECTOR type in the NUMERIC_STD package. A STD_LOGIC_VECTOR signal's value must first be converted into unsigned and then into integer, because there is no direct way to convert a STD_LOGIC_VECTOR signal's value into integer. **Figure 7** shows the steps required to convert a STD_LOGIC_VECTOR signal value into integer and vice versa [1]. In the to_unsigned() function (**Figure 7, INTEGER → UNSIGNED conversion**) the 'LENGTH is called an attribute. The B 'LENGTH expression is used to specify the length of signal B.

Signal definitions : signal A : STD_LOGIC_VECTOR(N-1 DOWNT0 0); signal B : UNSIGNED(N-1 DOWNT0 0); signal C : INTEGER;
STD_LOGIC_VECTOR → UNSIGNED conversion : Method : type casting. B <= UNSIGNED(A);
UNSIGNED → INTEGER conversion : Method : use of the “to_integer()” function of the NUMERIC_STD package. C <= to_integer(B);
INTEGER → UNSIGNED conversion : Method : use of the “to_unsigned()” function of the NUMERIC_STD package. B <= to_unsigned(C,N); OR B <= to_unsigned(C,B'LENGTH);
UNSIGNED → STD_LOGIC_VECTOR conversion : Method : type casting. A <= STD_LOGIC_VECTOR(B);

Figure 7

In lines 41-46 (**Figure 6**) the concatenate operator, &, is used to assign the value of a group of signals to a signal. For example in line 41 the most significant bit (lsl_op(N-1)) of the lsl_op signal is assigned with the value of A(N-2) and the least significant bit (lsl_op(0)) is assigned with the value '0', because the concatenate operator groups the signal values in this order.

In lines 48-65 (**Figure 6**) a process statement is used. A process statement is a concurrent statement and can be used like any other concurrent statement in the architecture body [2]. All concurrent statements can be optionally tagged (see line 48). This statement describes a multiplexer. The select signal of the multiplexer is the S_OP signal and its other inputs are the signals that hold the result of each operation (defined in lines 35-46). Multiplexer's output is the output signal RES of the alu_n entity.

The expression (unsigned(B) > unsigned(A)) compares the values of signals A and B as unsigned numbers. The unsigned conversion is used because the “>” operator is not defined for

signals of the `STD_LOGIC_VECTOR` type in the `NUMERIC_STD` package and because the desirable comparison must be done considering A and B signals as unsigned numbers.

Instead of the `NUMERIC_STD` package, the `STD_LOGIC_ARITH` and the `STD_LOGIC_UNSIGNED` packages could be used. The `STD_LOGIC_ARITH` package defines two signal types, `SIGNED` and `UNSIGNED`. These types are identical to the `STD_LOGIC_VECTOR` type because they represent an array of `STD_LOGIC` signals. The purpose of the `SIGNED` and `UNSIGNED` types is to allow the designer to indicate in the VHDL code what kind of number representation is being used. The `SIGNED` type is used in code for circuits that deal with signed (2's complement) numbers, and the `UNSIGNED` type is used in code that deals with unsigned numbers. The `STD_LOGIC_UNSIGNED` package specifies that `STD_LOGIC_VECTOR` signals should be treated like `UNSIGNED` signals. Similarly, a `STD_LOGIC_SIGNED` package specifies that `STD_LOGIC_VECTOR` signals should be treated like `SIGNED` signals. The `STD_LOGIC_ARITH` package, and hence the `STD_LOGIC_UNSIGNED` and `STD_LOGIC_SIGNED` packages, are not actually a part of the VHDL standards. They are provided by Synopsys Inc., which is a vendor of CAD software. However, these packages are included with most CAD systems that support VHDL, and they are widely used in practice [2]. **Figure 8** shows the changes that must be done in the code of **Figure 6** when the `STD_LOGIC_ARITH` and the `STD_LOGIC_UNSIGNED` packages are used.

Replace	With
<code>use IEEE.NUMERIC_STD.ALL;</code>	<code>use IEEE.STD_LOGIC_ARITH.ALL;</code> <code>use IEEE.STD_LOGIC_UNSIGNED.ALL;</code>
<code>add_op <=</code> <code>std_logic_vector(to_unsigned(to_integer(unsigned(A))</code> <code>+ to_integer(unsigned(tmp_b)) + cin,N+1));</code>	<code>add_op <=</code> <code>conv_std_logic_vector(conv_integer(A) +</code> <code>conv_integer(tmp_b) + cin,N+1);</code>
<code>bgta <= '1' when (unsigned(B) > unsigned(A)) else '0';</code>	<code>bgta <= '1' when (B > A) else '0';</code>

Figure 8

5. Behavioral simulation of the `a1u_n` module :

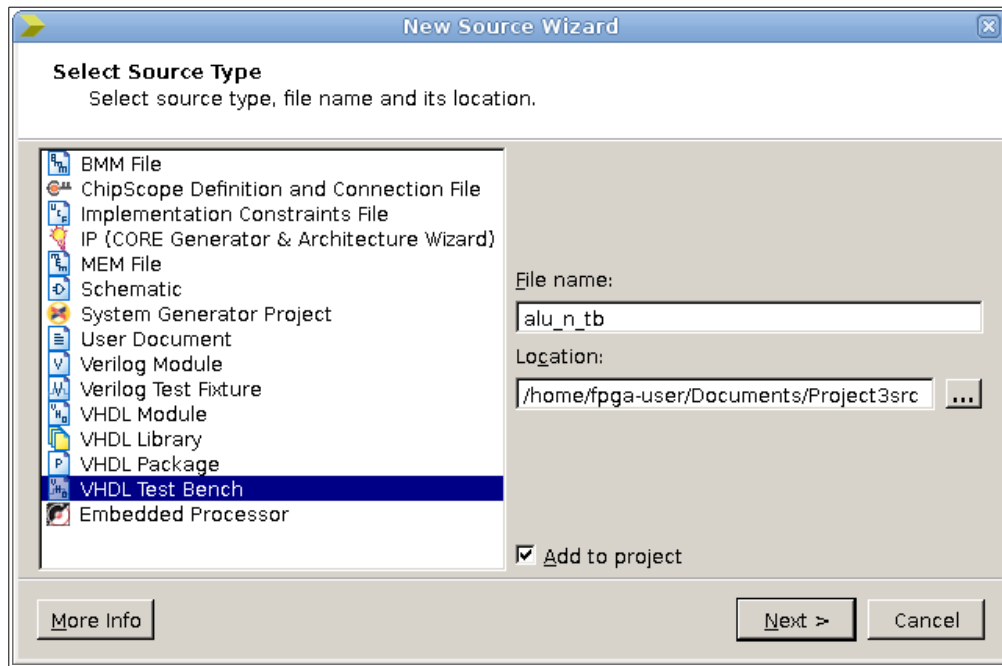


Figure 9

In the ISE Project Navigator window select Project->New Source.... In the New Source Wizard window type `alu_n_tb` in the File Name field, select VHDL Test Bench and click Next (see Figure 9). In the next New Source Wizard window associate the `alu_n_tb` file with the `alu_n` module, click Next and then click Finish to create the `alu_n_tb.vhd` testbench file. Modify the `alu_n_tb.vhd` testbench file to look like the one in Figure 10.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY alu_n_tb IS
5  END alu_n_tb;
6
7  ARCHITECTURE behavior OF alu_n_tb IS
8      -- Component Declaration for the Unit Under Test (UUT)
9      COMPONENT alu_n
10         PORT(
11             A : IN  std_logic_vector(15 downto 0);
12             B : IN  std_logic_vector(15 downto 0);
13             S_OP : IN  std_logic_vector(3 downto 0);
14             RES : OUT std_logic_vector(15 downto 0);
15             COUT : OUT std_logic;
16             VOUT : OUT std_logic
17         );
18     END COMPONENT;
19     --Inputs
20     signal A : std_logic_vector(15 downto 0) := (others => '0');
21     signal B : std_logic_vector(15 downto 0) := (others => '0');
22     signal S_OP : std_logic_vector(3 downto 0) := (others => '0');
23     --Outputs
24     signal RES : std_logic_vector(15 downto 0);
25     signal COUT : std_logic;
26     signal VOUT : std_logic;
27 BEGIN
28     -- Instantiate the Unit Under Test (UUT)
29     uut: alu_n PORT MAP (
30         A => A,
31         B => B,
32         S_OP => S_OP,
33         RES => RES,
34         COUT => COUT,
35         VOUT => VOUT
36     );
37     -- Stimulus process
38     stim_proc: process
39     begin
40         A <= X"7C05";
41         B <= X"7D0A";
42         S_OP <= "0000";
43         wait for 50 ns;
44         S_OP <= "0001";
45         wait for 50 ns;
46         S_OP <= "0010";
47         wait for 50 ns;
48         S_OP <= "0011";
49         wait for 50 ns;
50         S_OP <= "0100";
51         wait for 50 ns;
52         S_OP <= "0101";
53         wait for 50 ns;
54         S_OP <= "0110";
55         wait for 50 ns;
56         S_OP <= "0111";
57         wait for 50 ns;
58         S_OP <= "1000";
59         wait for 50 ns;
60         S_OP <= "1001";
61         wait for 50 ns;
62         S_OP <= "1010";
63         wait for 50 ns;
64         S_OP <= "1011";
65         wait for 50 ns;
66         S_OP <= "1100";
67         wait for 50 ns;
68         S_OP <= "1101";
69         wait for 50 ns;
70         S_OP <= "1110";
71         wait for 50 ns;
72         S_OP <= "1111";
73         wait;
74     end process;
75 END;

```

Figure 10

Statement in lines 40-41 (**Figure 10**) assign values to A and B signals using the hexadecimal value representation. Signals A and B carry these values until the end of the simulation.

In the ISE Project Navigator window select Simulation, select `alu_n_tb` testbench file, expand ISim Simulator and double-click Behavioral Check Syntax to check `alu_n_tb` testbench's syntax (see **Figure 11**).

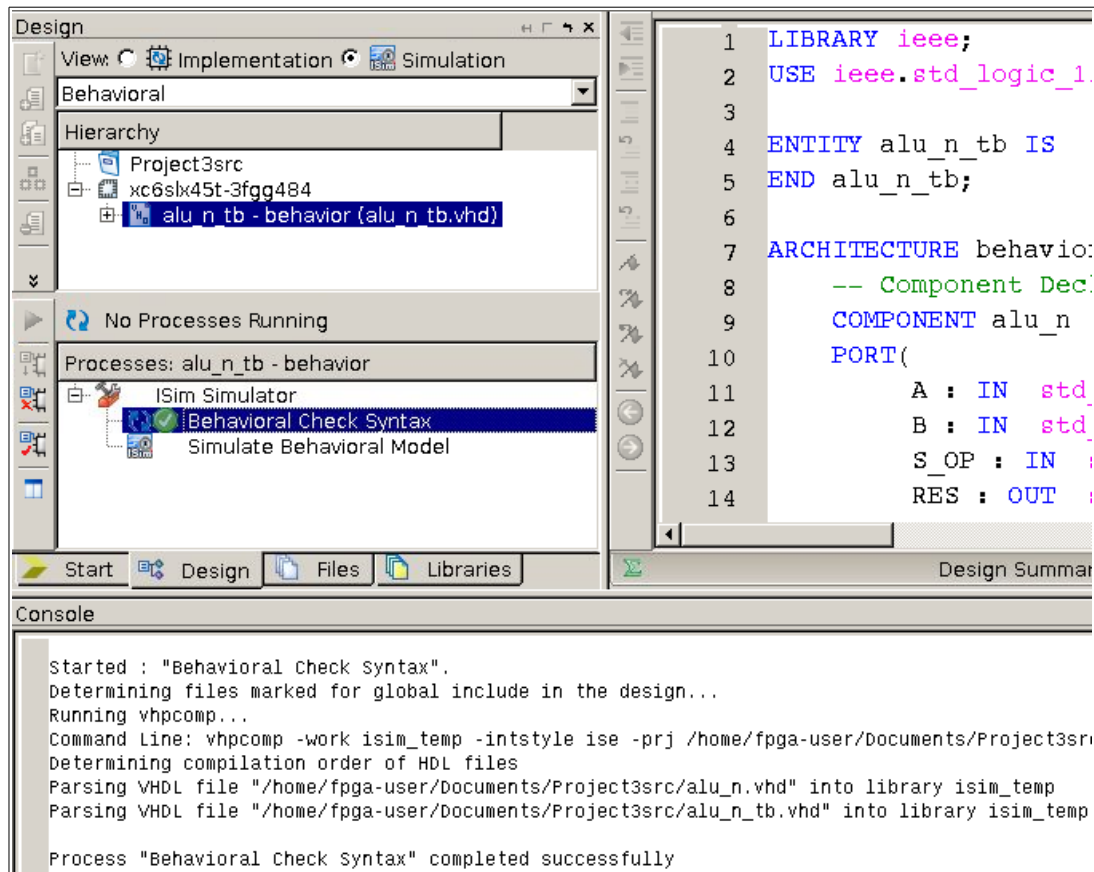


Figure 11


Right-click **Simulate Behavioral Model** and select **Process Properties**. Change **Simulation Run Time** to 800 ns and click OK. Now double-click **Simulate Behavioral Model** to run the simulation as specified by the `alu_n_tb` testbench file and the **ISim Simulation Run Time** parameter. Select **View->Zoom->To Full View** in **ISim** simulator window. Right-click on signals **A**, **B** and **RES** and select **Radix** to change the representation radix (first to **Unsigned Decimal** and then to **Signed Decimal**). Click on the waveform to verify the right execution of addition and subtraction (see **Figure 12**).

In **Figure 12**, a 2's complement overflow is generated during addition ($V_{OUT} = '1'$). This is correct because **A** and **B** represent positive numbers (in 2's complement form) and the result of the addition is negative in 2's complement form (bottom waveform in **Figure 12**). A carry is generated during subtraction ($C_{OUT} = '1'$). This is also correct because **B** is larger than **A** and that means that a borrow is used to perform the subtraction (see the upper waveform in **Figure 12**). The borrow is equal to 2^{16} and the result of the subtraction for the upper waveform in **Figure 12** can be interpreted as follows : $RES = (A + 2^{16}) - B$. The subtraction result in 2's complement form is correct and a 2's complement overflow is not generated.

Right-click on signals **A**, **B**, and **RES** and select **Radix->Binary** to check the results of the remaining operations.

Close the **ISim** simulator window.

Radix : Unsigned Decimal

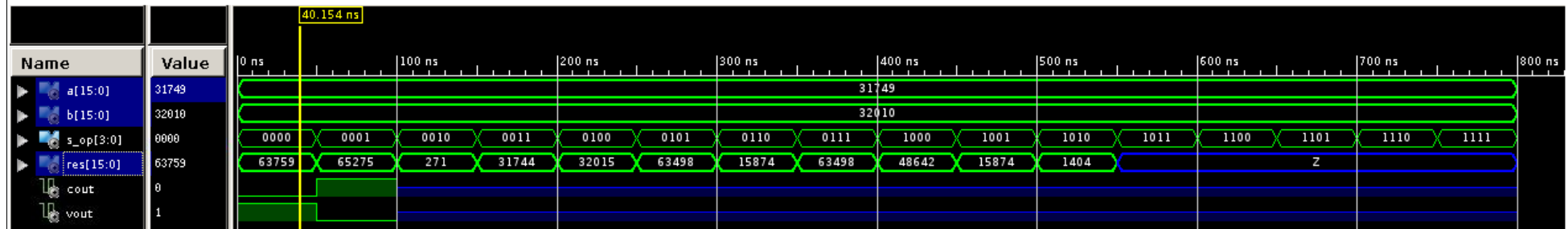

Radix : Signed Decimal

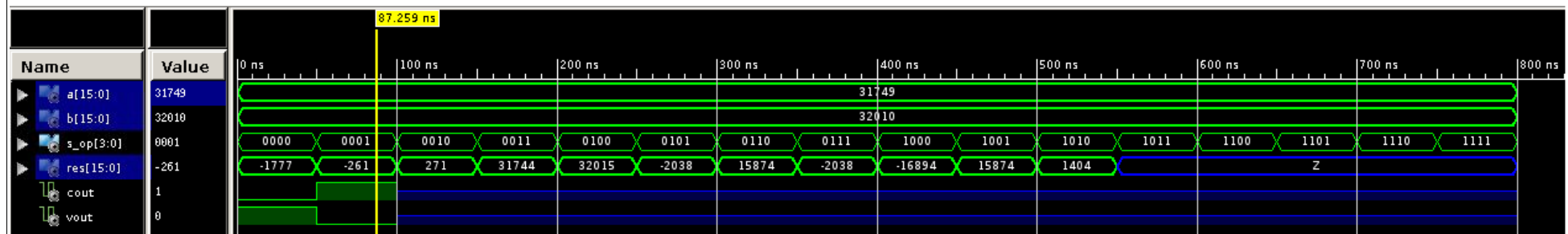


Figure 12

6. Generate ICON and VIO cores :

In the ISE Project Navigator window, select Project->New Source.... In the New Source Wizard window, type `icon_mod` in the File Name field, select IP (CORE Generator & Architecture Wizard) and click Next (see **Figure 13**).

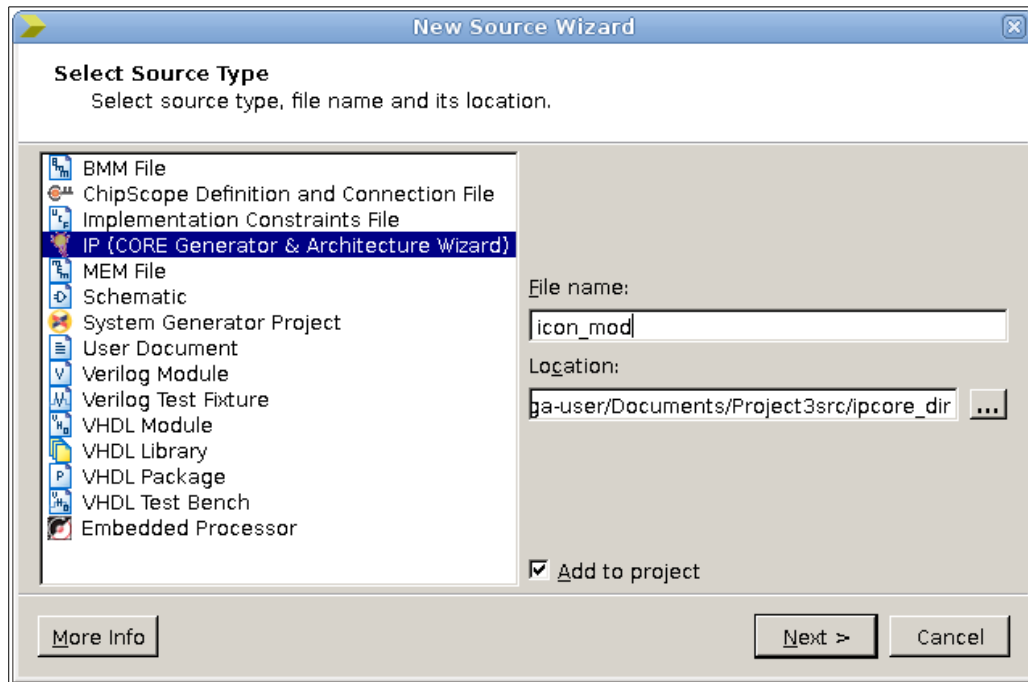


Figure 13

In the New Source Wizard window (Select IP), check Only IP compatible with chosen part, expand Debug & Verification, expand ChipScope Pro, select ICON (ChipScope Pro - Integrated Controller) version 1.06.a, click Next and Finish (see **Figure 14**).

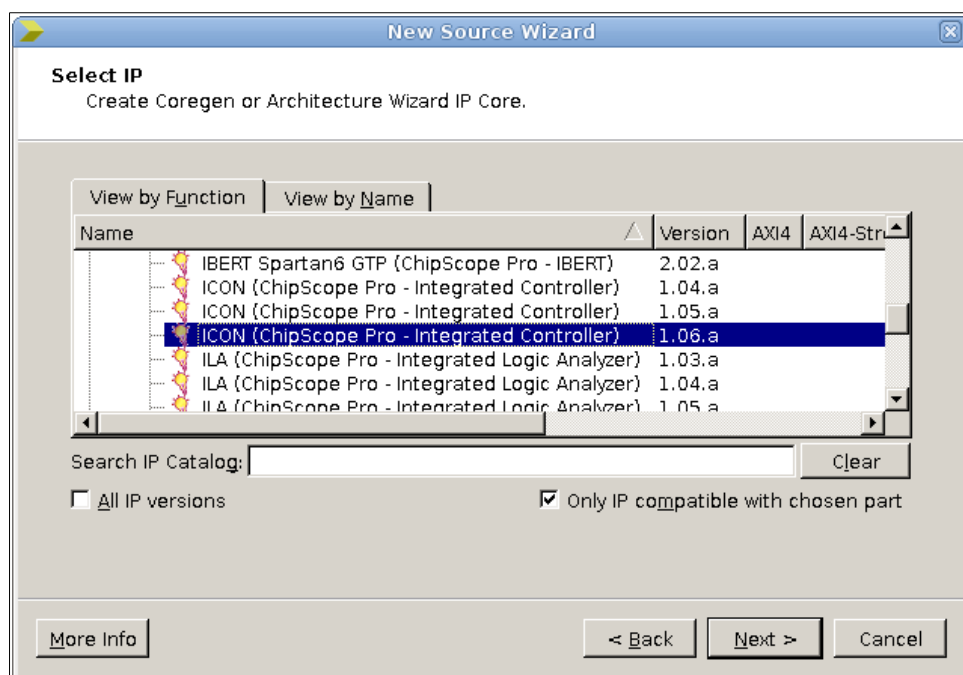



Figure 14

In the ICON (ChipScope Pro - Integrated Controller) window click Generate.

In the ISE Project Navigator window, select Project->New Source.... In the New Source Wizard window type `vio_mod` in the File Name field, select IP (CORE Generator & Architecture Wizard) and click Next.

In the New Source Wizard window (Select IP), check Only IP compatible with chosen part, expand Debug & Verification, expand ChipScope Pro, select VIO (ChipScope Pro - Virtual Input/Output) version 1.05.a, click Next and Finish.

In the VIO (ChipScope Pro - Virtual Input/Output) window, check Enable Asynchronous Input Port (Width 18), check Enable Asynchronous Output Port (Width 36) and click Generate (see **Figure 15**). The VIO output port will feed the `alu_n` module input ports (16-bit A + 16-bit B + 4-bit `S_OP` = 36 bits) and the VIO input port will read the `alu_n` module output port (16-bit RES + 1-bit COUT +1-bit VOUT = 18 bits).

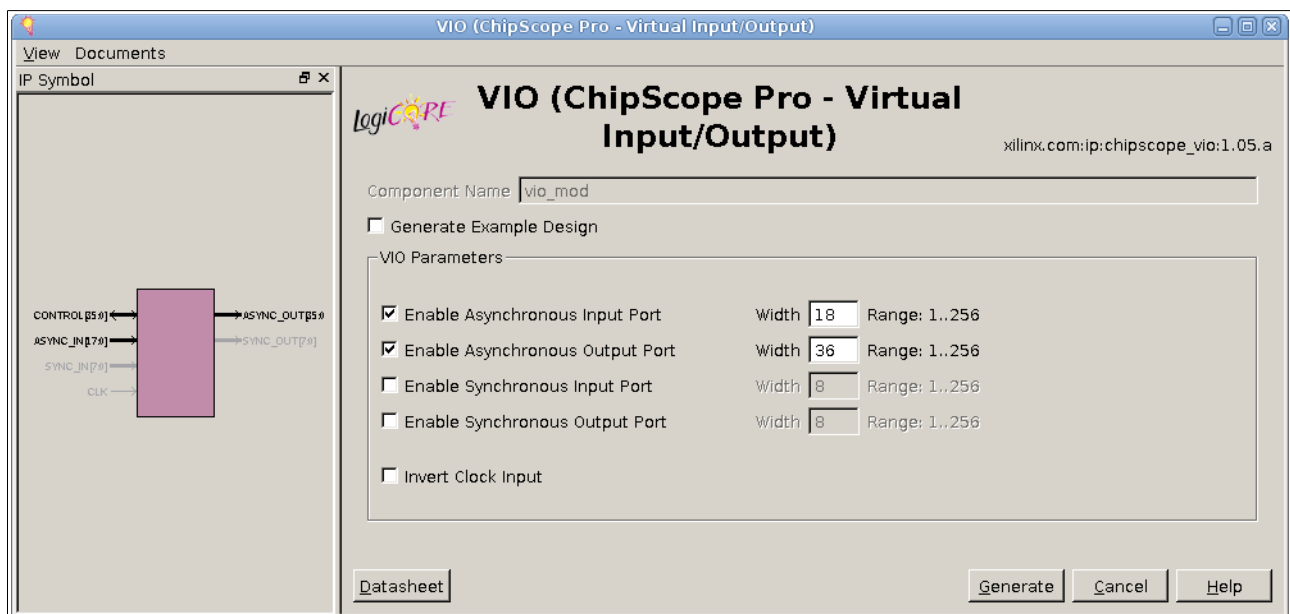**Figure 15**

The `alu_n` module and the two cores (ICON and VIO) will be used as components in a single VHDL module (`alu_n_vio` module - top-module). The implementation of `alu_n_vio` module will be used in ChipScope Pro Analyzer for `alu_n` module verification [3], [4].

7. Create and Define the structure of the `alu_n_vio` VHDL module :

In the ISE Project Navigator window, select Project->New Source.... In the New Source Wizard window type `alu_n_vio` in the File Name field, select VHDL Module and click Next. In the next New Source Wizard window (Define Module) change the Architecture name field from Behavioral to Structural, click Next and Finish.

Module `alu_n_vio` doesn't have any ports (no ports were defined in module creation) because no FPGA general purpose I/O ports will be used for `alu_n` module verification. JTAG Boundary Scan (BSCAN) dedicated FPGA ports will be used (through the ICON core – the ICON core provides an interface between the JTAG Boundary Scan (BSCAN) component of the FPGA and the VIO core) [3].

In the ISE Project Navigator window, select Implementation, select the `icon_mod` core, expand CORE Generator and double-click View HDL Instantiation Template. Copy the component declaration of the `icon_mod` core in the `alu_n_vio` module's architecture declarative region. Copy the instance declaration of the `icon_mod` core in the `alu_n_vio` module's architecture body and name the instance `part1`. Follow the above-mentioned steps for `vio_mod` core instantiation in the `alu_n_vio` module and name the instance `part2`.

Copy the entity declaration of the `alu_n` module to the `alu_n_vio` module's architecture declarative region and edit it (in the `alu_n_vio` module) to form the component declaration of the `alu_n` module. **Figure 16** shows how to complete `alu_n_vio` module's description.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity alu_n_vio is
5  end alu_n_vio;
6
7  architecture Structural of alu_n_vio is
8      -- ICON icon_mod component declaration.
9      component icon_mod
10         PORT (
11             CONTROL0 : INOUT STD_LOGIC_VECTOR(35 DOWNTO 0));
12         end component;
13      -- VIO vio_mod component declaration.
14      component vio_mod
15         PORT (
16             CONTROL : INOUT STD_LOGIC_VECTOR(35 DOWNTO 0);
17             ASYNC_IN : IN STD_LOGIC_VECTOR(17 DOWNTO 0);
18             ASYNC_OUT : OUT STD_LOGIC_VECTOR(35 DOWNTO 0));
19         end component;
20      -- mux_2_1_8 component declaration.
21      component alu_n is
22         generic(N : integer := 16);
23         Port(A,B : in STD_LOGIC_VECTOR(N-1 DOWNTO 0);
24             S_OP : in STD_LOGIC_VECTOR(3 DOWNTO 0);
25             RES : out STD_LOGIC_VECTOR(N-1 DOWNTO 0);
26             COUT : out STD_LOGIC;
27             VOUT : out STD_LOGIC);
28         end component;
29      -- Declaration of signals for internal connections.
30      signal CONTROL : STD_LOGIC_VECTOR(35 DOWNTO 0);
31      signal ASYNC_IN : STD_LOGIC_VECTOR(17 DOWNTO 0);
32      signal ASYNC_OUT : STD_LOGIC_VECTOR(35 DOWNTO 0);
33  begin
34      -- ICON icon_mod instantiation.
35      part1 : icon_mod
36         port map (CONTROL0 => CONTROL);
37      -- VIO vio_mod instantiation.
38      part2 : vio_mod
39         port map (
40             CONTROL => CONTROL,
41             ASYNC_IN => ASYNC_IN,
42             ASYNC_OUT => ASYNC_OUT);
43      part3 : alu_n
44         port map (
45             A => ASYNC_OUT(15 downto 0),
46             B => ASYNC_OUT(31 downto 16),
47             S_OP => ASYNC_OUT(35 downto 32),
48             RES => ASYNC_IN(15 downto 0),
49             COUT => ASYNC_IN(16),
50             VOUT => ASYNC_IN(17));
51  end Structural;

```

Figure 16

In the ISE Project Navigator window, select Implementation, right-click on `alu_n_vio` module and select Select as Top Module, select the `alu_n_vio` module, expand Synthesize – XST and double-click Check Syntax to ensure `alu_n_vio` module's

correctness.

8. Synthesize and Implement the `alu_n_vio` design :

In the ISE Project Navigator window select Implementation, select the `alu_n_vio` module, expand Synthesize – XST and double-click View RTL Schematic to view the RTL schematic of the synthesized `alu_n_vio` module. In the Set RTL/Tech Viewer Startup Mode select Start with a Schematic of the top-level block and click OK. Double-click on the synthesized `alu_n_vio` module (black-box-like) graphic to view the schematic shown in Figure 17.

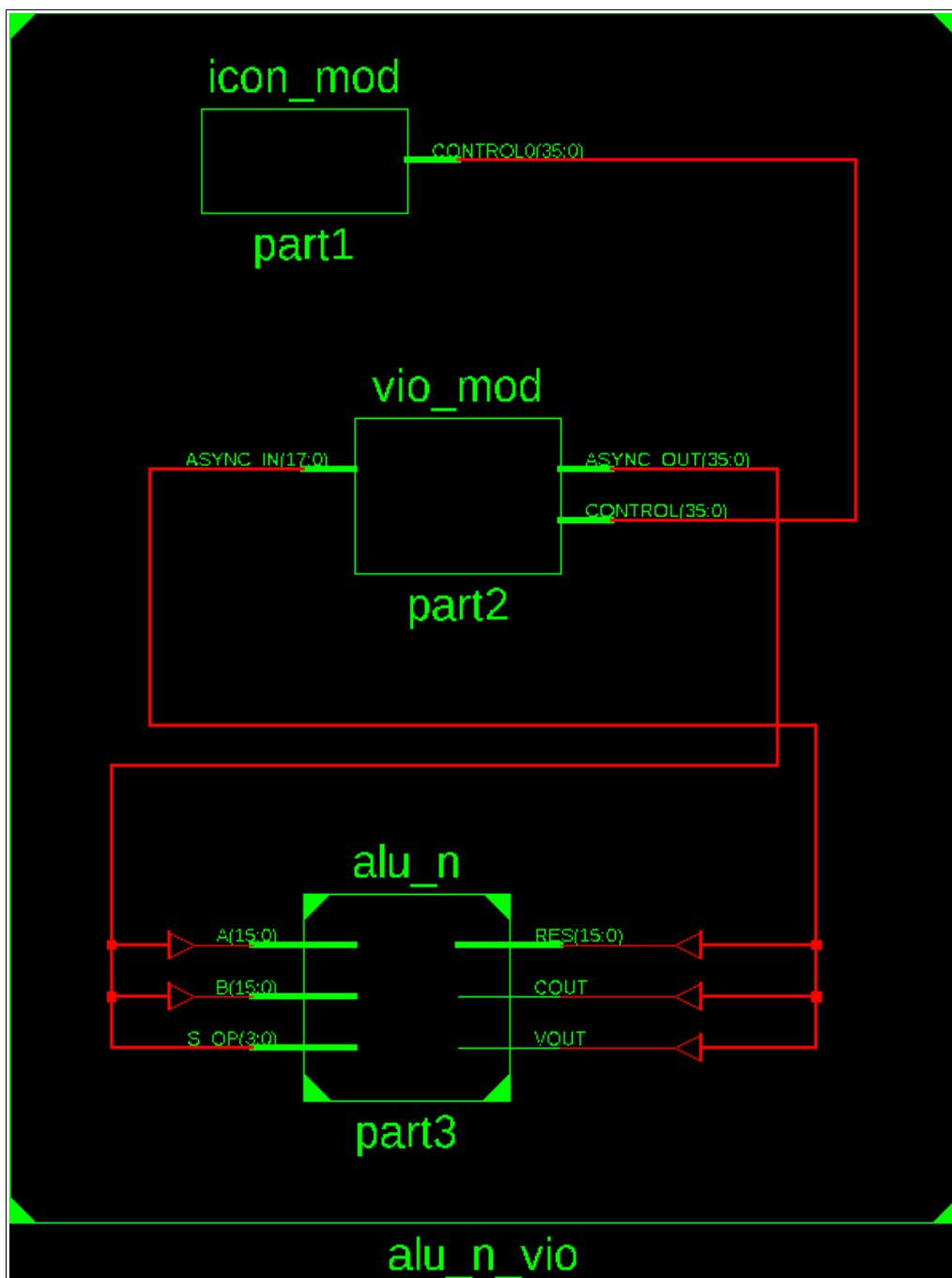
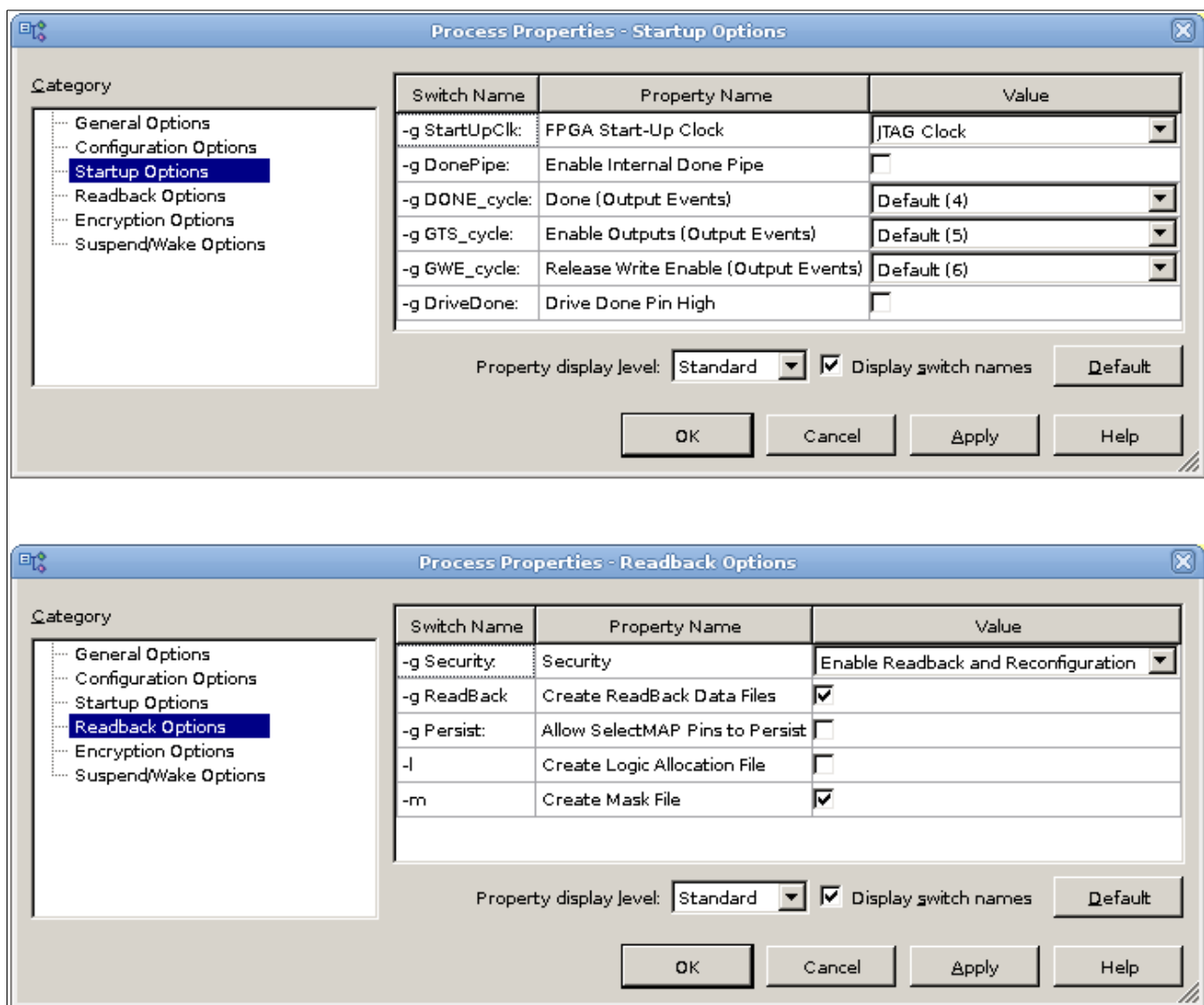


Figure 17

To implement the `alu_n_vio` module, in the ISE Project Navigator window select Implementation, select the `alu_n_vio` module and double-click Implement Design.

9. Generate Programming (Configuration) File :

In the ISE Project Navigator window select Implementation, select the `alu_n_vio` module, right-click Generate Programming File and select Process Properties. In the Process Properties – Startup Options window select Startup Options category and change FPGA Start-Up Clock property to JTAG Clock, then select Readback Options category and check Create Readback Data files and Create Mask File properties (see **Figure 18**). Click OK to close the Process Properties – Startup Options window. The above changes have been made in order to program the FPGA and verify FPGA programming using JTAG.

**Figure 18**

Double-click Generate Programming File to complete programming file generation.

10. Configure the FPGA :

In the ISE Project Navigator window select Implementation, select the `alu_n_vio` module, double-click Configure Target Device and click OK to open Impact. Impact software tool is used for FPGA configuration. In the ISE iMPACT window double-click Boundary Scan.

Right-click on Right click to Add Device or Initialize JTAG chain and select Initialize Chain. Click Yes to the Auto Assign Configuration Files Query Dialog, select Bypass for the xcace device, navigate to `/home/fpga-user/Documents/Project3src`, select the `alu_n_vio.bit` file and click Open for the xc6slx45t Spartan-6 FPGA. Click No to the Attach SPI or BPI PROM window. Select Device 2 in the Device Programming Properties window and check the Verify property. Right-click on the xc6slx45t Spartan-6 FPGA and select Program (see **Figure 19**).

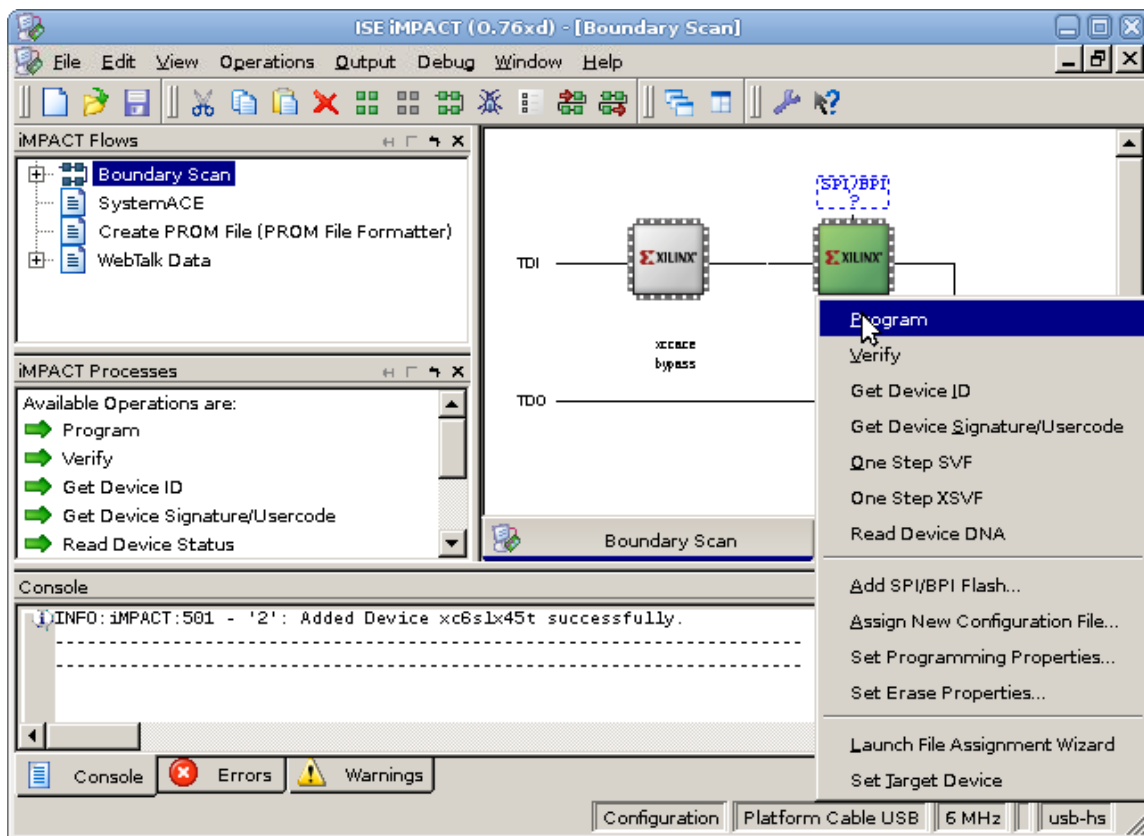


Figure 19

After the Program Succeeded message close the ISE iMPACT window (click No to iMPACT-Save Project window).

11. Analyze design using ChipScope :

In the ISE Project Navigator window select Implementation, select the `alu_n_vio` module and double-click Analyze Design Using ChipScope. Click the Open Cable/Search JTAG Chain icon under the File menu in ChipScope Pro Analyzer window (see **Figure 20**) and click OK to the ChipScope Pro Analyzer (JTAG Chain Device Order)

window.

 


Figure 20

Double-click the VIO Console (see Figure 21) to open it.

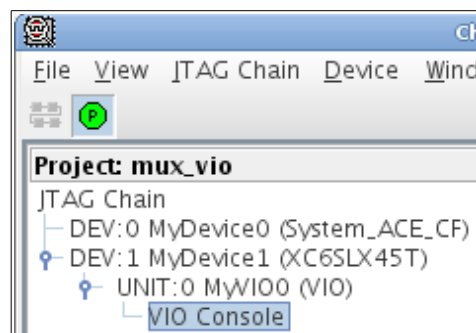


Figure 21

Select signals AsyncIn[0] to [15], right-click on them and select Move to Bus->New Bus. Right-click on the newly created AsyncIn bus, select Rename and type RES to the Input window. Right-click on the AsyncIn[16] signal, select Rename and type COUT to the Input window. Right-click on the AsyncIn[17] signal, select Rename and type VOUT to the Input window. Select signals AsyncOut[0] to [15], right-click on them and select Move to Bus->New Bus. Right-click on the newly created AsyncOut bus, select Rename and type A to the Input window. Select signals AsyncOut[16] to [31], right-click on them and select Move to Bus->New Bus. Right-click on the newly created AsyncOut_1 bus, select Rename and type B to the Input window. Select signals AsyncOut[31] to [35], right-click on them and select Move to Bus->New Bus. Right-click on the newly created AsyncOut_2 bus, select Rename and type S_OP to the Input window.

Right-click on each bus and select the desired radix (Bus Radix). Give values to A, B and S_OP buses and observe the alu_n module outputs. Figure 22 shows the execution of the A XOR B operation.

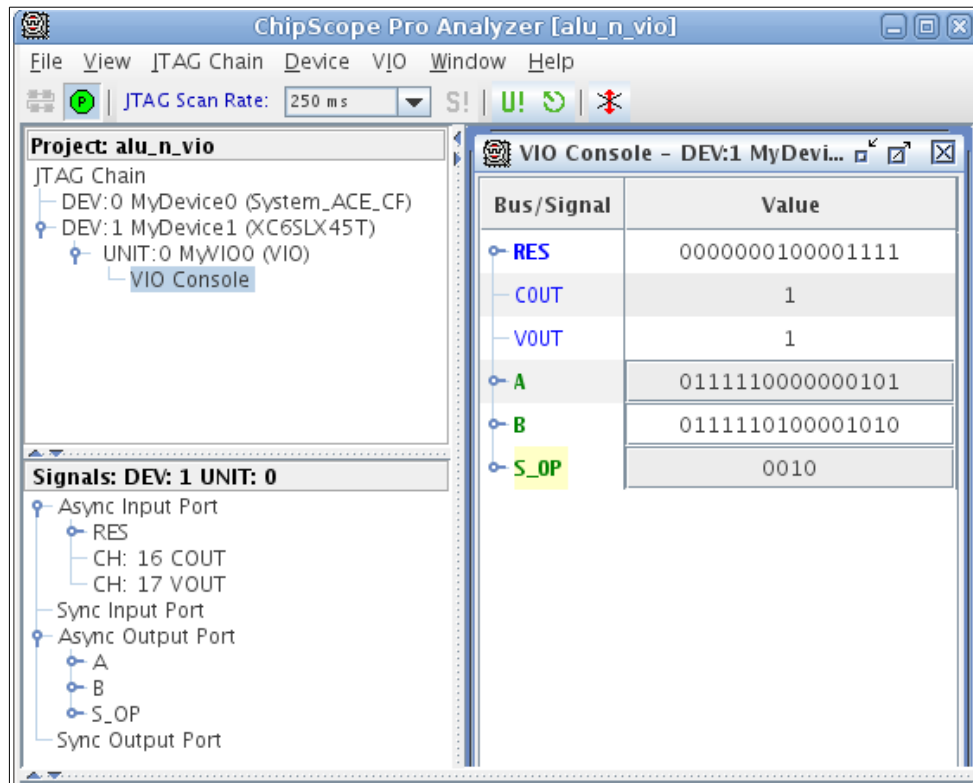


Figure 22

The COUT and VOUT outputs don't carry the 'Z' value as they were supposed to; they carry the logic value '1' instead. This is due a synthesis warning that states : WARNING:Xst:2042 - Unit alu_n: 18 internal tristates are replaced by logic (pull-up yes): COUT, RES<0>, RES<10>, RES<11>, RES<12>, RES<13>, RES<14>, RES<15>, RES<1>, RES<2>, RES<3>, RES<4>, RES<5>, RES<6>, RES<7>, RES<8>, RES<9>, VOUT. This warning is generated because the Spartan-6 configurable logic blocks (CLBs) don't have internal tristate buffers [5]. So all the tristate buffers in the design are converted to logic that behaves consistently ('Z' is replaced by '1'). If the alu_n module was implemented using general purpose FPGA pins, this warning would not have been generated because the Spartan-6 input/output blocks (IOBS) contain tristate buffers [6].

References

- [1] Edwin Naroska, comp.lang.vhdl Frequently Asked Questions And Answers, <http://www.vhdl.org/comp.lang.vhdl/>
- [2] Stephen Brown and Zvonko Vranesic, Fundamentals of Digital Logic with VHDL Design, 3rd Edition, McGraw-Hill, 2009
- [3] Xilinx Corporation, LogiCORE IP ChipScope Pro Integrated Controller (ICON) (v1.05a), 2011, <http://www.xilinx.com>
- [4] Xilinx Corporation, LogiCORE IP ChipScope Pro Virtual Input/Output (VIO) (1.04a), 2011,

<http://www.xilinx.com>

[5] Xilinx Corporation, Spartan-6 FPGA Configurable Logic Block User Guide, 2010,
<http://www.xilinx.com>

[6] Xilinx Corporation, Spartan-6 FPGA SelectIO Resources User Guide, 2010,
<http://www.xilinx.com>